

**AB04**  
**Common Emitter NPN**  
**Transistor Characteristics**

**Operating Manual**  
**Ver.1.1**

An ISO 9001 : 2000 company



94-101, Electronic Complex Pardesipura,  
Indore- 452010, India

Tel : 91-731- 2570301/02, 4211100

Fax: 91- 731- 2555643

e mail : [info@scientech.bz](mailto:info@scientech.bz)

Website : [www.scientech.bz](http://www.scientech.bz)

Toll free : 1800-103-5050



# CERTIFICATE

The Certification Body for  
Quality Management Systems  
of TÜV Rheinland India Pvt. Ltd.

certifies in accordance with  
TÜV Rheinland Group procedures that

## Scientech Technologies Pvt. Ltd.

Unit-1: 94-101, Electronics Complex, Pardeshi Pura,  
Indore – 452 010, Madhya Pradesh, India

Unit-2: 90-91, Electronics Complex, Pardeshi Pura,  
Indore – 452 010, Madhya Pradesh, India

has established and applies a quality management system for

**Design, Manufacture of Electronic Test & Measuring  
Instruments, Training Products for Electrical & Electronics  
Education and Providing Technology Training**

An audit was performed, Report No. 07930

Proof has been furnished that the requirements according to

**DIN EN ISO 9001: 2000**

are fulfilled.

The certificate is valid until 2010-11-20

Certificate Registration No. **85 100 001 07930**



A handwritten signature in black ink, likely of a representative of the certification body.

Bangalore, 2007-11-21

The validity of this certificate is subject to timely completion of Surveillance audits as agreed  
in the Contract. The Validity of the Certificate can be verified under [WWW.tuv.com](http://WWW.tuv.com) with the Identification No. 9105027653

The certification Body of  
TÜV Rheinland India Pvt. Ltd.

04/11/NABCB/00

[www.tuv.com](http://www.tuv.com)

**AB04**  
**Common Emitter NPN**  
**Transistor Characteristics**  
**Table of Contents**

<b>1.</b>	Introduction	4
<b>2.</b>	Theory	6
<b>3.</b>	Experiments	8
	Experiment 1	8
	Study of the characteristics of NPN transistor in Common Emitter configuration and to evaluate Input Resistance, Output Resistance and Current Gain	
<b>4.</b>	Data Sheet	14
<b>5.</b>	Warranty	16
<b>6.</b>	List of Accessories	16

**RoHS Compliance**



Scientech Products are RoHS Complied.

RoHS Directive concerns with the restrictive use of Hazardous substances (Pb, Cd, Cr, Hg, Br compounds) in electric and electronic equipments.

Scientech products are “Lead Free” and “Environment Friendly”.

It is mandatory that service engineers use lead free solder wire and use the soldering irons upto (25 W) that reach a temperature of 450°C at the tip as the melting temperature of the unleaded solder is higher than the leaded solder.

### **Introduction**

**AB04** is a compact, ready to use **Transistor Characteristics** experiment board. This is useful for students to plot different characteristics of NPN transistor in common base configuration and to understand various region of operation of PNP transistor. It can be used as stand alone unit with external DC power supply or can be used with **Sciencetech Analog Lab ST2612** which has built in DC power supply, AC power supply, function generator, modulation generator, continuity tester, toggle switches, and potentiometer.

### **List of Boards :**

<b>Model</b>	<b>Name</b>
<b>AB01</b>	Diode characteristics (Si, Zener, LED)
<b>AB02</b>	Transistor characteristics (CB NPN)
<b>AB03</b>	Transistor characteristics (CB PNP)
<b>AB05</b>	Transistor characteristics (CE PNP)
<b>AB06</b>	Transistor characteristics (CC NPN)
<b>AB07</b>	Transistor characteristics (CC PNP)
<b>AB08</b>	FET characteristics
<b>AB09</b>	Rectifier Circuits
<b>AB10</b>	Wheatstone bridge
<b>AB11</b>	Maxwell's Bridge
<b>AB12</b>	De Sauty's Bridge
<b>AB13</b>	Schering Bridge
<b>AB14</b>	Darlington Pair
<b>AB15</b>	Common Emitter Amplifier
<b>AB16</b>	Common Collector Amplifier
<b>AB17</b>	Common Base Amplifier
<b>AB18</b>	RC-Coupled Amplifier
<b>AB19</b>	Cascode Amplifier
<b>AB20</b>	Direct Coupled Amplifier
<b>AB21</b>	Class A Amplifier
<b>AB22</b>	Class B Amplifier (push pull emitter follower)
<b>AB23</b>	Class C Tuned Amplifier
<b>AB24</b>	Transformer Coupled Amplifier
<b>AB25</b>	Phase Locked Loop (FM Demodulator & Frequency Divider / Multiplier)
<b>AB26</b>	FET Amplifier
<b>AB27</b>	Voltage Controlled Oscillator
<b>AB28</b>	Multivibrator (Monostable / Astable)
<b>AB29</b>	F-V and V-F Converter
<b>AB30</b>	V-I and I-V Converter
<b>AB31</b>	Zener Voltage Regulator
<b>AB32</b>	Transistor Series Voltage Regulator
<b>AB33</b>	Transistor Shunt Voltage Regulator
<b>AB35</b>	DC Ammeter
<b>AB37</b>	DC Ammeter (0-2mA)
<b>AB39</b>	Instrumentation Amplifier

---

**AB04**

---

<b>AB41</b>	Differential Amplifier (Transistorized)
<b>AB42</b>	Operational Amplifier (Inverting / Non-inverting / Differentiator)
<b>AB43</b>	Operational Amplifier (Adder/Scalar)
<b>AB44</b>	Operational Amplifier (Integrator/ Differentiator)
<b>AB45</b>	Schmitt Trigger and Comparator
<b>AB49</b>	K Derived Filter
<b>AB51</b>	Active filters (Low Pass and High Pass)
<b>AB52</b>	Active Band Pass Filter
<b>AB54</b>	Tschebyscheff Filter
<b>AB56</b>	Fiber Optic Analog Link
<b>AB57</b>	Owen's Bridge
<b>AB58</b>	Anderson's Bridge
<b>AB59</b>	Maxwell's Inductance Bridge
<b>AB64</b>	RC – Coupled Amplifier with Feedback
<b>AB66</b>	Wien Bridge Oscillators
<b>AB67</b>	Colpitt Oscillator
<b>AB68</b>	Hartley Oscillator
<b>AB80</b>	RLC Series and RLC Parallel Resonance
<b>AB82</b>	Thevenin's and Maximum Power Transfer Theorem
<b>AB83</b>	Reciprocity and Superposition Theorem
<b>AB84</b>	Tellegen's Theorem
<b>AB85</b>	Norton's theorem
<b>AB88</b>	Diode Clipper
<b>AB89</b>	Diode Clampers
<b>AB90</b>	Two port network parameter
<b>AB91</b>	Optical Transducer (Photovoltaic cell)
<b>AB92</b>	Optical Transducer (Photoconductive cell/LDR)
<b>AB93</b>	Optical Transducer (Phototransistor)
<b>AB96</b>	Temperature Transducer (RTD & IC335)
<b>AB97</b>	Temperature Transducer (Thermocouple)
<b>AB101</b>	DSB Modulator and Demodulator
<b>AB102</b>	SSB Modulator and Demodulator
<b>AB106</b>	FM Modulator and Demodulator

and many more.....

### **Theory**


Transistor characteristics are the curves, which represent relationship between different DC currents and voltages of a transistor. These are helpful in studying the operation of a transistor when connected in a circuit. The three important characteristics of a transistor are:

1. Input characteristic.
2. Output characteristic.
3. Constant current transfer characteristic.

#### **Input Characteristic :**

In common emitter configuration, it is the curve plotted between the input current ( $I_B$ ) verses input voltage ( $V_{BE}$ ) for various constant values of output voltage ( $V_{CE}$ ).

The approximated plot for input characteristic is shown in figure 1. This characteristic reveal that for fixed value of output voltage  $V_{CE}$ , as the base to emitter voltage increases, the emitter current increases in a manner that closely resembles the diode characteristics.

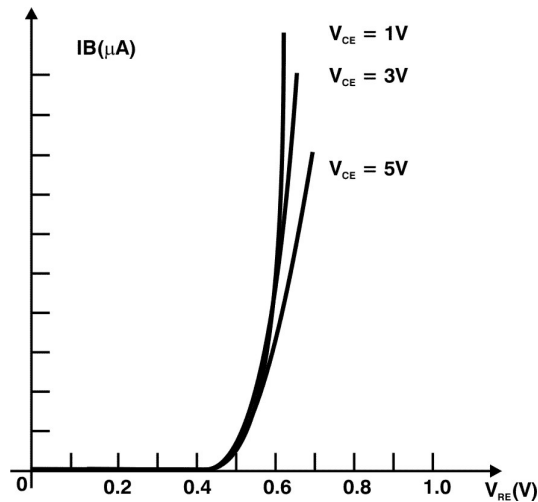

**Figure 1**

### Output Characteristic :

This is the curve plotted between the output current  $I_C$  versus output voltage  $V_{CE}$  for various constant values of input current  $I_B$ .

The output characteristic has three basic region of interest as indicated in figure 2 the active region, cutoff region and saturation region.

In active region the collector base junction is reverse biased while the base emitter junction is forward biased. This region is normally employed for linear (undistorted) amplifier.

In cutoff region the collector base junction and base emitter junction of the transistor both are reverse biased. In this region transistor acts as an 'Off' switch.

In saturation region the collector base junction and base emitter junction of the transistor both are forward biased. In this region transistor acts as an on switch.

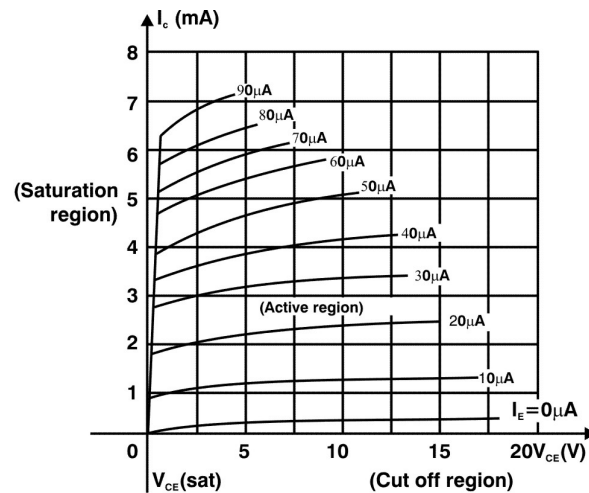


Figure 2

### Constant current transfer Characteristics :

This is the curve plotted between output collector current  $I_C$  versus input base current  $I_B$  for constant value of output voltage  $V_{CE}$ .

The approximated plot for this characteristic is shown in figure 3.

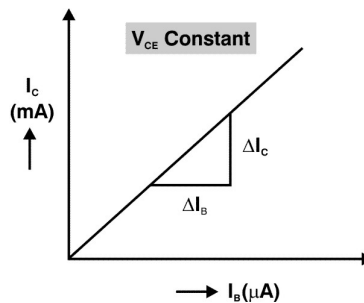


Figure 3

### Experiment

**Objective :**

**Study of the characteristics of NPN transistor in common emitter configuration and to evaluate :**

1. Input resistance
2. Output resistance
3. Current gain

**Equipments Needed :**

1. Analog board of **AB04**.
2. DC power supplies +12V, +5V from external source or **ST2612 Analog Lab**.
3. Digital Multimeter (3 numbers).
4. 2 mm patch cords.

**Circuit diagram :**

Circuit used to plot different characteristics of transistor is shown in figure 4.

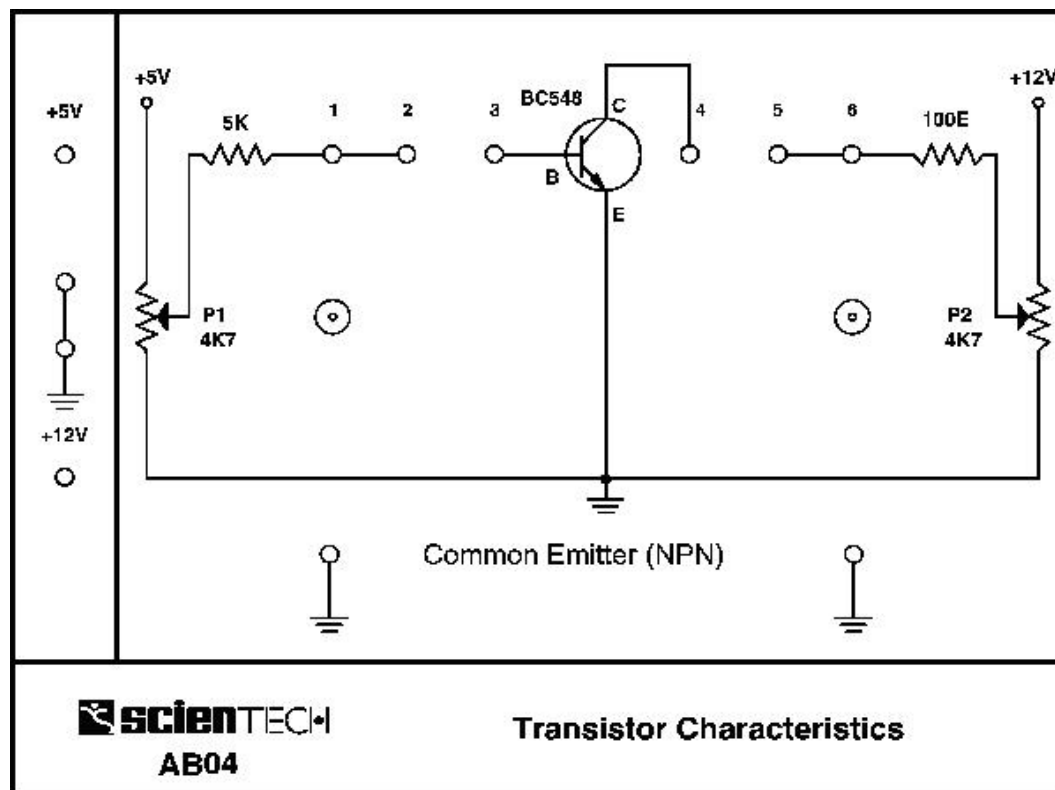


Figure 4



**Procedure :**

- Connect +5V and +12V DC power supplies at their indicated position from external source or **ST2612 Analog Lab**.
- To plot input characteristics proceed as follows :
  1. Rotate both the potentiometer  $P_1$  and  $P_2$  fully in CCW (counter clockwise direction).
  2. Connect Ammeter between test point 2 and 3 to measure input base current  $I_B(\mu A)$ .
  3. Short or connect a 2mm patch cord between test point 4 and 5.
  4. Connect one voltmeter between test point 1 and ground to measure input voltage  $V_{BE}$  other voltmeter between test point 6 and ground to measure output voltage  $V_{CE}$ .
  5. Switch 'On' the power supply.
  6. Vary potentiometer  $P_2$  and set a value of output voltage  $V_{CE}$  at some constant value (1V, 3V...)
  7. Vary the potentiometer  $P_1$  so as to increase the value of input voltage  $V_{BE}$  from zero to 0.8V in step and measure the corresponding values of input current  $I_B$  for different constant value of output voltage  $V_{CE}$  in an observation Table 1.
  8. Rotate potentiometer  $P_1$  fully in CCW direction.
  9. Repeat the procedure from step 6 for different sets of output voltage  $V_{CE}$ .
  10. Plot a curve between input voltage  $V_{BE}$  and input current  $I_B$  as shown in figure 1 using suitable scale with the help of Observation Table 1. This curve is the required input characteristic.

Observation Table 1 :

S. no.	Input voltage $V_{BE}$	Input current $I_B$ (mA) at constant value of output voltage		
		$V_{CE} = 1V$	$V_{CE} = 3V$	$V_{CE} = 5V$
1.	0.0V			
2.	0.1V			
3.	0.2V			
4.	0.3V			
5.	0.4V			
6.	0.5V			
7.	0.6V			
8.	0.7V			
9.	0.8V			

- To plot output characteristics proceed as follows:
  1. Switch 'Off' the power supply.
  2. Rotate both the potentiometer  $P_1$  and  $P_2$  fully in CCW (counter clockwise direction).
  3. Connect voltmeter between test point 6 and ground to measure output voltage  $V_{CE}$ .
  4. Connect one Ammeter between test point 2 and 3 to measure input current  $I_B$ ( $\mu A$ ) and other Ammeter between test point 4 and 5 to measure output current  $I_C$ (mA).
  5. Switch 'On' the power supply.
  6. Vary potentiometer  $P_1$  and set a value of input current  $I_B$  at some constant value (0 $\mu A$ , 10 $\mu A$ .....100 $\mu A$ )
  7. Vary the potentiometer  $P_2$  so as to increase the value of output voltage  $V_{CE}$  from zero to maximum value in step and measure the corresponding values of output current  $I_C$  for different constant value of input current  $I_B$  in an observation table2.
  8. Rotate potentiometer  $P_2$  fully in CCW direction.
  9. Repeat the procedure from step 6 for different sets of input current  $I_B$ .
  10. Plot a curve between output voltage  $V_{CE}$  and output current  $I_C$  as shown in figure 2 using suitable scale with the help of Observation Table 2. This curve is the required output characteristic.

Observation Table 2 :

S. No.	Output voltage $V_{CE}$	Output current $I_C$ (mA) at constant value of input current				
		$I_B = 0\text{mA}$	$I_B = 10\text{mA}$	$I_B = 20\text{mA}$	$I_B = 30\text{mA}$	$I_B = 40\text{mA}$
1.	0.0V					
2.	0.5V					
3.	1.0V					
4.	2.0V					
5.	3.0V					
6.	4.0V					
7.	5.0V					
8.	6.0V					
9.	7.0V					
10.	8.0V					

- To plot constant current transfer characteristics proceed as follows:
  1. Switch 'Off' the power supply.
  2. Rotate both the potentiometer  $P_1$  and  $P_2$  fully in CCW (counter clockwise direction).
  3. Connect voltmeter between test point 6 and ground to measure output voltage  $V_{CE}$ .
  4. Connect one Ammeter between test point 2 and 3 to measure input current  $I_B$  (mA) and other Ammeter between test point 4 and 5 to measure output current  $I_C$  (mA).
  5. Switch 'On' the power supply.
  6. Vary potentiometer  $P_2$  and set a value of output voltage  $V_{CE}$  at maximum value.
  7. Vary the potentiometer  $P_1$  so as to increase the value of input current  $I_B$  from zero to 10mA in step and measure the corresponding values of output current  $I_C$  in an Observation Table 3.
  8. Plot a curve between output current  $I_C$  and input current  $I_B$  as shown in figure 3 using suitable scale with the help of observation Table 3. This curve is the required Transfer characteristic.

**Observation Table 3 :**

<b>S. No.</b>	<b>Input current <math>I_B</math> (mA)</b>	<b>Output Current <math>I_c</math> (Ma) At Constant Output Voltage <math>V_{ce}</math> = Maximum</b>
<b>1.</b>	00.0 $\mu$ A	
<b>2.</b>	10.0 $\mu$ A	
<b>3.</b>	20.0 $\mu$ A	
<b>4.</b>	30.0 $\mu$ A	
<b>5.</b>	40.0 $\mu$ A	
<b>6.</b>	50.0 $\mu$ A	
<b>7.</b>	60.0 $\mu$ A	
<b>8.</b>	70.0 $\mu$ A	
<b>9.</b>	80.0 $\mu$ A	
<b>10.</b>	90.0 $\mu$ A	
<b>11.</b>	100.0 $\mu$ A	

**Calculations :**

1. **Input resistance :** It is the ratio of change in the input voltage  $V_{BE}$  to change in the input current  $I_B$  at constant value of output voltage  $V_{CE}$  or it is the reciprocal of the slope obtained from the input characteristic.

**Mathematically :**

$$R_{in} \frac{1}{\text{Slope from Input characteristics}} = \frac{1}{\Delta I_B / \Delta V_{BE}} = \frac{\Delta V_{BE}}{\Delta I_B \text{ at constant } V_{CB}}$$

To calculate input resistance determine the slope from the input characteristic curve obtained from observation Table 1. Reciprocal of this slope will give the required input resistance.

2. **Output resistance :** It is the ratio of change in the output voltage  $V_{CE}$  to change in the output current  $I_C$  at constant value of input current  $I_B$  or it is the reciprocal of the slope obtained from the output characteristic.

**Mathematically :**

$$R_{in} \frac{1}{\text{Slope from Input characteristics}} = \frac{1}{\Delta I_C / \Delta V_{CE}} = \frac{\Delta V_{CE}}{\Delta I_C \text{ at constant } I_B}$$

To calculate output resistance determine the slope from the output characteristic curve obtained from observation Table 2. Reciprocal of this slope will give the required output resistance.

3. **Current gain :** It is the ratio of change in the output current  $I_C$  to change in the input current  $I_B$  at constant value of output voltage  $V_{CE}$  or it is the slope obtained from the constant current transfer characteristic. It is denoted by  $\beta_{ac}$

**Mathematically :**

$$b_{ac} = \text{Slope of constant current transfer characteristic} = \frac{\Delta I_C}{\Delta I_B}$$

To calculate current gain, determine the slope from the constant current transfer characteristic curve obtained from observation Table 3. This slope is the required current gain.

**Results :**

Input resistance  $R_{in} =$  \_\_\_\_\_

Output resistance  $R_{out}$  \_\_\_\_\_ =


Current Gain  $\beta_{ac} =$  \_\_\_\_\_

## Data Sheet

## BC546/547/548/549/550
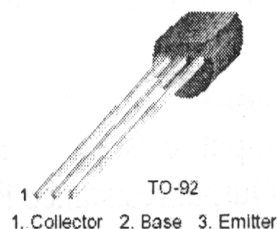
## Switching and Applications

- High Voltage: BC546,  $V_{CE0}=65V$
- Low Noise: BC549, BC550
- Complement to BC556 ... BC560



## NPN Epitaxial Silicon Transistor

Absolute Maximum Ratings  $T_a=25^{\circ}C$  unless otherwise noted

Symbol	Parameter	Value	Units
$V_{CBO}$	Collector-Base Voltage : BC546	80	V
	: BC547/550	50	V
	: BC548/549	30	V
$V_{CEO}$	Collector-Emitter Voltage : BC546	65	V
	: BC547/550	45	V
	: BC548/549	30	V
$V_{EBO}$	Emitter-Base Voltage : BC546/547	6	V
	: BC548/549/550	5	V
$I_C$	Collector Current (DC)	100	mA
$P_C$	Collector Power Dissipation	500	mW
$T_J$	Junction Temperature	150	$^{\circ}C$
$T_{STG}$	Storage Temperature	-65 ~ 150	$^{\circ}C$

Electrical Characteristics  $T_a=25^{\circ}C$  unless otherwise noted

Symbol	Parameter	Test Condition	Min.	Typ.	Max.	Units
$I_{CBO}$	Collector Cut-off Current	$V_{CB}=30V, I_E=0$			15	nA
$h_{FE}$	DC Current Gain	$V_{CE}=5V, I_C=2mA$	110		800	
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C=10mA, I_B=0.5mA$		90	250	mV
		$I_C=100mA, I_B=5mA$		200	600	mV
$V_{BE(sat)}$	Base-Emitter Saturation Voltage	$I_C=10mA, I_B=0.5mA$		700		mV
		$I_C=100mA, I_B=5mA$		900		mV
$V_{BE(on)}$	Base-Emitter On Voltage	$V_{CE}=5V, I_C=2mA$	580	660	700	mV
		$V_{CE}=5V, I_C=10mA$			720	mV
$f_T$	Current Gain Bandwidth Product	$V_{CE}=5V, I_C=10mA, f=100MHz$		300		MHz
$C_{ob}$	Output Capacitance	$V_{CB}=10V, I_E=0, f=1MHz$		3.5	6	pF
$C_{ib}$	Input Capacitance	$V_{EB}=0.5V, I_C=0, f=1MHz$		9		pF
NF	Noise Figure : BC546/547/548 : BC549/550	$V_{CE}=5V, I_C=200\mu A$		2	10	dB
		$f=1KHz, R_G=2K\Omega$		1.2	4	dB
		$V_{CE}=5V, I_C=200\mu A$		1.4	4	dB
		$R_G=2K\Omega, f=30\sim 15000MHz$		1.4	3	dB

 $h_{FE}$  Classification

Classification	A	B	C
$h_{FE}$	110 ~ 220	200 ~ 450	420 ~ 800

## Typical Characteristics

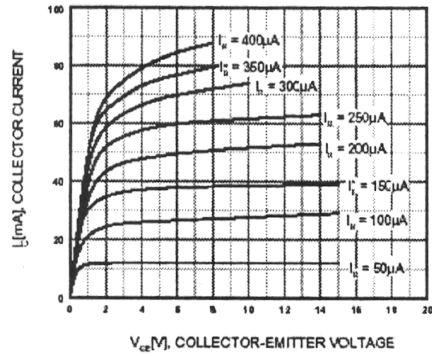


Figure 1. Static Characteristic

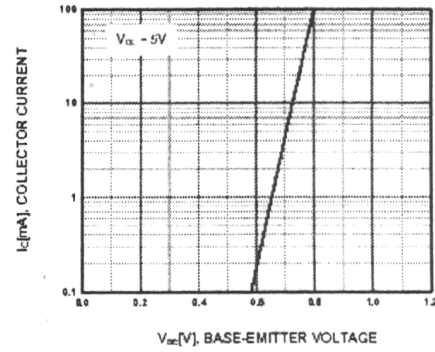


Figure 2. Transfer Characteristic

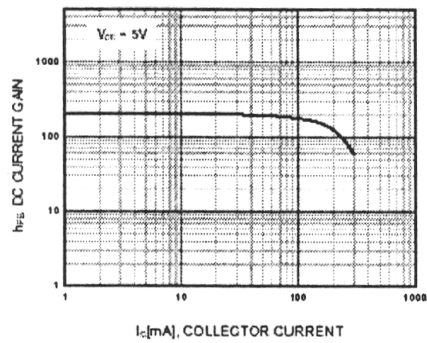


Figure 3. DC current Gain

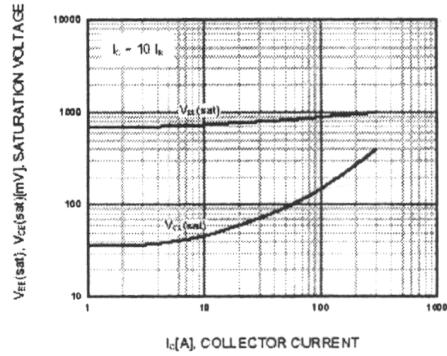
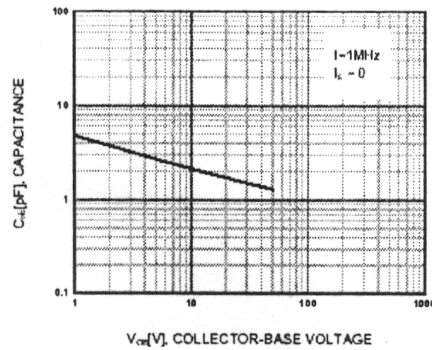
Figure 4. Base-Emitter Saturation Voltage  
Collector-Emitter Saturation Voltage

Figure 5. Output Capacitance

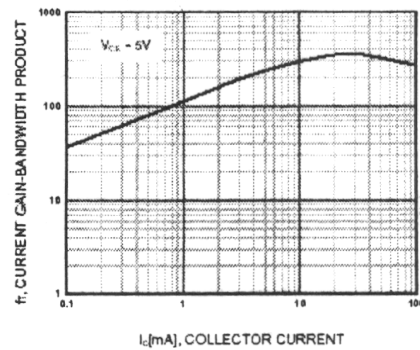


Figure 6. Current Gain Bandwidth Product

### **Warranty**

1. We guarantee the product against all manufacturing defects for 24 months from the date of sale by us or through our dealers. Consumables like dry cell etc. are not covered under warranty.
2. The guarantee will become void, if
  - a) The product is not operated as per the instruction given in the operating manual.
  - b) The agreed payment terms and other conditions of sale are not followed.
  - c) The customer resells the instrument to another party.
  - d) Any attempt is made to service and modify the instrument.
3. The non-working of the product is to be communicated to us immediately giving full details of the complaints and defects noticed specifically mentioning the type, serial number of the product and date of purchase etc.
4. The repair work will be carried out, provided the product is dispatched securely packed and insured. The transportation charges shall be borne by the customer.

For any Technical Problem Please Contact us at [service@scientech.bz](mailto:service@scientech.bz)

### **List of Accessories**

1. 2 mm Patch Cords (Red) ..... 2 Nos.
2. 2 mm Patch Cord (Black) ..... 2 Nos.
3. 2 mm Patch Cord (Blue) ..... 1 No.
4. e-Manual ..... 1 No.

Updated 08-01-2009