AB08 N-Channel FET Characteristics

> Operating Manual Ver.1.1

An ISO 9001 : 2000 company



94-101, Electronic Complex Pardesipura, Indore- 452010, India Tel : 91-731- 2570301/02, 4211100 Fax: 91- 731- 2555643 e mail : info@scientech.bzWebsite : www.scientech.bz Toll free : 1800-103-5050



## AB08 N-Channel FET Characteristics

## **Table of Contents**

1.	Introduction	4
2.	Theory	6
3.	Experiments	8
	• Experiment 1 Study of the characteristics of JFET (Junction field effect transistor) in common source configuration and evaluation of:	10
4.	Data Sheet	15
5.	Warranty	17
6.	List of Accessories	17

## **RoHS Compliance**



Scientech Products are RoHS Complied.

RoHS Directive concerns with the restrictive use of Hazardous substances (Pb, Cd, Cr, Hg, Br compounds) in electric and electronic equipments.

Scientech products are "Lead Free" and "Environment Friendly".

It is mandatory that service engineers use lead free solder wire and use the soldering irons upto (25 W) that reach a temperature of  $450^{\circ}$ C at the tip as the melting temperature of the unleaded solder is higher than the leaded solder.

#### Introduction

**AB08** is a compact, ready to use **FET Characteristics** experiment board. This is useful for students to plot different characteristics of an N channel Field Effect Transistor and to understand operation of an FET in different regions. It can be used as stand alone unit with external DC power supply or can be used with **Scientech Analog Lab ST2612** which has built in DC power supply, AC power supply, function generator, modulation generator, continuity tester, toggle switches, and potentiometer. **List of Boards :** 

Model	Name
AB01	Diode characteristics (Si, Zener, LED)
AB02	Transistor characteristics (CB NPN)
AB03	Transistor characteristics (CB PNP)
<b>AB04</b>	Transistor characteristics (CE NPN)
AB05	Transistor characteristics (CE PNP)
AB06	Transistor characteristics (CC NPN)
<b>AB07</b>	Transistor characteristics (CC PNP)
AB09	Rectifier Circuits
<b>AB10</b>	Wheatstone bridge
AB11	Maxwell's Bridge
AB12	De Sauty's Bridge
AB13	Schering Bridge
<b>AB14</b>	Darlington Pair
AB15	Common Emitter Amplifier
<b>AB16</b>	Common Collector Amplifier
<b>AB17</b>	Common Base Amplifier
<b>AB18</b>	RC-Coupled Amplifier
AB19	Cascode Amplifier
AB20	Direct Coupled Amplifier
AB21	Class A Amplifier
AB22	Class B Amplifier (push pull emitter follower)
AB23	Class C Tuned Amplifier
AB24	Transformer Coupled Amplifier
AB25	Phase Locked Loop (FM Demodulator & Frequency Divider /
4.0.20	Multiplier)
AB26	FET Amplifier
AB27	Voltage Controlled Oscillator
AB28 AB29	Multivibrator (Monostable / Astable) F-V and V-F Converter
AB29 AB30	V-I and I-V Converter
AB30 AB31	Zener Voltage Regulator
AB31 AB32	Transistor Series Voltage Regulator
AB32 AB33	Transistor Shunt Voltage Regulator
AB35 AB35	DC Ammeter
AB33 AB37	DC Ammeter (0-2mA)
	Lestrementation Amerilifican

AB08	
AB41	Differential Amplifier (Transistorized)
<b>AB42</b>	Operational Amplifier (Inverting / Non-inverting / Differentiator)
AB43	Operational Amplifier (Adder/Scalar)
<b>AB44</b>	Operational Amplifier (Integrator/ Differentiator)
<b>AB45</b>	Schmitt Trigger and Comparator
AB49	K Derived Filter
AB51	Active filters (Low Pass and High Pass)
<b>AB52</b>	Active Band Pass Filter
<b>AB54</b>	Tschebyscheff Filter
AB56	Fiber Optic Analog Link
<b>AB57</b>	Owen's Bridge
<b>AB58</b>	Anderson's Bridge
AB59	Maxwell's Inductance Bridge
<b>AB64</b>	RC – Coupled Amplifier with Feedback
AB66	Wien Bridge Oscillators
<b>AB67</b>	Colpitt Oscillator
AB68	Hartley Oscillator
AB80	RLC Series and RLC Parallel Resonance
AB82	Thevenin's and Maximum Power Transfer Theorem
AB83	Reciprocity and Superposition Theorem
<b>AB84</b>	Tellegen's Theorem
AB85	Norton's theorem
<b>AB88</b>	Diode Clipper
<b>AB89</b>	Diode Clampers
AB90	Two port network parameter
AB91	Optical Transducer (Photovoltaic cell)
AB92	Optical Transducer (Photoconductive cell/LDR)
AB93	Optical Transducer (Phototransistor)
AB96	Temperature Transducer (RTD & IC335)
AB97	Temperature Transducer (Thermocouple)
AB101	DSB Modulator and Demodulator
AB102	SSB Modulator and Demodulator
AB106	FM Modulator and Demodulator
	and many more


#### Theory

FET is a voltage controlled current device so its characteristics are the curves which represent relationship between different DC currents and voltages. These are helpful in studying different region of operation of a Field effect transistor when connected in a circuit. The two important characteristics of a Field Effect Transistor are:

- **1.** Output /Drain characteristic.
- 2. Transfer characteristic.
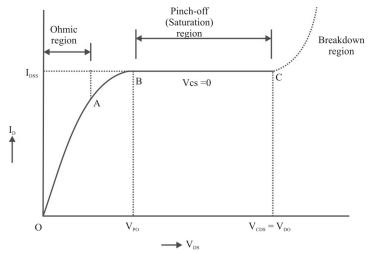
## **Output / Drain Characteristics :**

It is the curve plotted between output drain current  $I_D$  versus output drain to source voltage  $V_{DS}$  for constant values of input Gate to source voltage  $V_{GS}$  as shown in figure 1.





It can be subdivided into following four regions:

## **Ohmic region OA :**

This part of the characteristic is linear indicating that for low values of  $V_{DS}$ , current varies directly with voltage following Ohm's Law. It means that JFET behaves like an ordinary resistor till point A (called knee) is reached.

## Curve AB :

In this region,  $I_D$  increases at inverse square law rate upto point B which is called Pinch-off point. This progressive fall in the rate of increase of  $I_D$  is caused by the square law increase in the depletion region at each gate up to point B where the two regions are closest without touching each other. The drain to source voltage  $V_{DS}$ corresponding to point B is called pinch-off voltage  $V_{PO}$ .

## **Pinch-off region BC :**

It is also known as saturation region or 'amplifier' region. Here, JFET operates as a constant-current device because  $I_D$  is relatively independent of  $V_{DS}$ . It is due to the fact that as  $V_{DS}$  increases channel resistance also increases proportionally thereby keeping  $I_D$  practically constant at  $I_{DSS}$ .

Drain current in this region is given by Shockley's equation

It is the normal operating region of the JFET when used as an amplifier.

$$I_{D} = I_{DSS} [1 - (V_{GS} / V_{PO})^{2}] = I_{DSS} [- (V_{GS} / V_{GS (off)})^{2}]$$

### **Breakdown region :**

If  $V_{DS}$  is increased beyond its value corresponding to point C (called avalanche breakdown voltage), JFET enters the breakdown region where  $I_D$  increases to an extensive value. This happens because the reversed biased gate channel PN junction undergoes avalanche breakdown when small change in  $V_{DS}$  produce very large change in  $I_D$ .

## JFET characteristics with External Bias :

Figure 2 shows a family of  $I_D$  versus  $V_{DS}$  curves for different values of  $V_{GS}$ . It is seen that as the negative gate bias voltage is increased:

Pinch-off voltage  $V_P$  is reached at a lower value of  $V_{DS}$  than  $V_{GS} = 0$ . Value of  $V_{DS}$  for breakdown is decreased.


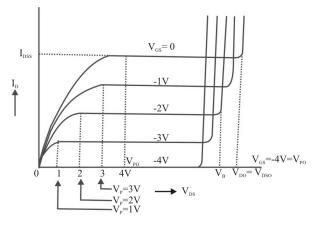


Figure 2
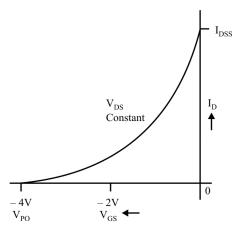
#### **Transfer Characteristic :**

It is the curve plotted between output drain current versus input Gate to source voltage for constant values of output drain to source voltage as shown in figure 3.



#### Figure 3

It is similar to the transconductance characteristics of a vacuum tube or a transistor. It shows that when  $V_{GS} = 0$ ,  $I_D = I_{DSS}$  and when  $I_D = 0$ ,  $V_{GS} = V_{PO}$ . The transfer characteristic approximately follows the equation

$$I_{D} = I_{DSS} [1 - (V_{GS} / V_{PO})^{2}] = I_{DSS} [1 - (V_{GS} / V_{GS(off)})^{2}]$$

The above equation can be written as  $V_{GS} = V_{GS \text{ (off)}} [1 - (I_D / I_{DSS})^{1/2}]$  These characteristics can also be obtained from the drain/output characteristics by reading off  $V_{GS}$  and  $I_{DSS}$  values for different values of  $V_{DS}$ .

The various parameters of a JFET can be obtained from its two characteristics.

The main parameters of a JFET when connected in common source mode are

#### AC Drain Resistance, r<sub>d</sub>:

It is the AC resistance between drain and source terminals when JFET is operating in the pinch-off region. It is given by

$$r_d = change in V_{DS}$$
 at  $V_{GS}$  constant or  $r_d = V_{DS} / I_D | V_{GS}$   
change in  $I_D$ 

An alternative name is dynamic drain resistance. It is given by the slope of the drain characteristics in the pinch off region. It is sometimes written as  $r_{ds}$  emphasizing the fact that it is the resistance from drain to source. Since  $r_d$  is usually the output resistance of a JFET, it may also be expressed as an output admittance  $y_{os}$ . Obviously,  $y_{os} = 1/r_d$ . It has a very high value.

#### Transconductance, g<sub>m</sub>:

It is simply the slope of transfer characteristics

 $g_m = \underline{change \ in \ } I_D \quad at \ V_{DS} \ constant \ or \ r_d = I_D \ / \ V_{GS} \ | \ V_{DS} \ change \ in \ V_{GS}$ 

Its unit is siemens (S) /Mho. It is also called forward transconductance  $(g_{fs})$  or forward transadmittance  $Y_{fs}$ . The transconductance measured at  $I_{DSS}$  is written as  $g_{mo}$ .

Mathematically

$$g_{\rm m} = g_{\rm mo} \left[ 1 - (V_{\rm GS} / V_{\rm P}) \right]$$

#### **Amplification factor, m:**

It is given by

$$\mu = \underline{\text{change in } V_{DS}} \quad \text{at } I_D \text{ constant or } \mu = V_{DS} / V_{GS} | I_{DS} \\ \underline{\text{change in } V_{GS}}$$

It can be proved from above that  $\mu = g_m \times r_d = g_{fs} \times r_d$ 

## DC drain resistance, R<sub>DS</sub> :

It is also called the static or ohmic resistance of the channel. It is given by

$$R_{DS} = V_{DS} / I_D$$

## Experiment

**Objective :** 

Study of the characteristics of JFET (Junction field effect transistor) in common source configuration and evaluation of:


- 1. AC drain resistance
- 2. Transconductance
- **3.** Amplification factor
- 4. Drain Resistance

**Equipments Needed :** 

- 1. Analog board of **AB08**.
- 2. DC power supplies +12V,-5V from external source or ST2612 Analog Lab.
- **3.** Digital Multimeter (3 numbers).
- 4. 2 mm patch cords.
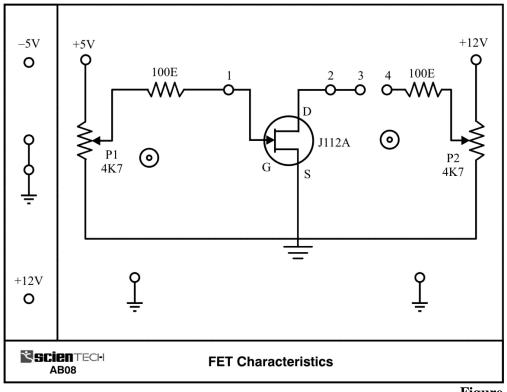
## **Circuit diagram :**

Circuit used to plot different characteristics of transistor is shown in figure 4.





## **Procedure :**

- 1. Connect -5V and + 12V DC power supplies at there indicated position from external source or ST2612 Analog Lab.
- 2. To plot Drain characteristics proceed as follows :
- **3.** Rotate both the potentiometer  $P_1$  and  $P_2$  fully in counter clockwise direction.
- 4. Connect Ammeter between test point 3 and 4 to measure output drain current  $I_D$  (mA).
- 5. Connect one voltmeter between test point 1 and ground to measure input voltage  $V_{GS}$  other voltmeter between test point 2 and ground to measure output voltage  $V_{DS}$ .
- 6. Switch 'On' the power supply.
- 7. Vary the potentiometer  $P_2$  so as to increase the value of output voltage  $V_{DS}$  from zero to 10V in step and measure the corresponding values of output drain current  $I_D$  for different constant value of output voltage  $V_{DS}$  in an observation table 1.
- 8. Rotate potentiometer P<sub>2</sub> fully in Counter Clockwise direction.
- **9.** Rotate potentiometer P<sub>1</sub> and set the value of input gate to source voltage at some constant value (-1V, -2V, -3V.....)
- 10. Repeat the procedure from step 6 for different sets of input voltage  $V_{GS}$ .
- 11. Plot a curve between output voltage  $V_{DS}$  and output current  $I_D$  at different constant values of input gate to source voltage as shown in figure 2 using suitable scale with the help of observation table 1. This curve is the required output/Drain characteristic.

### **Observation Table 1 :**

S. no.	Output voltage	Output Drain current I <sub>D</sub> (mA) at constant Va of input voltage				
	V <sub>DS</sub> (volt)	$V_{GS} = 0V$	$V_{GS} = -1V$	$V_{GS} = -2V$	$V_{GS} = -3V$	
1.	0.0V					
2.	1.0V					
3.	2.0V					
4.	3.0V					
5.	4.0V					
6.	5.0V					
7.	6.0V					
8.	7.0V					
9.	8.0V					
10.	9.0V					

- 1. To plot Transfer characteristics proceed as follows :
- 2. Switch 'Off' the power supply.
- **3.** Rotate both the potentiometer  $P_1$  and  $P_2$  fully in Counter Clockwise (counter clockwise direction).
- 4. Connect voltmeter between test point 6 and ground to measure output voltage  $V_{DS}$ .
- 5. Connect one Ammeter between test point 3 and 4 to measure output current  $I_{D}(mA)$
- 6. Vary potentiometer P<sub>2</sub> and set a value of output voltage V<sub>DS</sub> at some constant value (1 V, 2V, 3V.....)
- 7. Vary the potentiometer  $P_1$  so as to increase the value of input voltage  $V_{GS}$  from zero to maximum value in step and measure the corresponding values of output current  $I_D$  in an observation table 2
- 8. Rotate potentiometer P<sub>1</sub> fully in Counter Clockwise direction.
- 9. Repeat the procedure from step 5 for different sets of output voltage  $V_{DS}$ .
- 10. Plot a curve between input voltage  $V_{GS}$  and output current  $I_D$  as shown in Figure 3 using suitable scale with the help of observation table 2. This curve is the required Transfer characteristic.

## **Observation Table 2 :**

S. No.	Input voltage		t constant va	value of input		
	V <sub>GS</sub> (volt)	$V_{DS} = 1V$	$V_{DS} = 2V$	$V_{DS} = 3V$	$V_{DS} = 4V$	$V_{DS} = 5V$
1.	0.0V					
2.	-0.5V					
3.	-1.0V					
4.	-1.5V					
5.	-2.0V					
6.	-2.5V					
7.	-3.0V					
8.	-3.5V					
9.	-4.0V					

#### **Calculations :**

## AC Drain Resistance, r<sub>d</sub>:

It is the AC resistance between drain and source terminals when JFET is operating in the pinch-off region. To calculate AC drain resistance calculate the slope of the drain characteristics in the pinch off region obtained from Observation Table 1.

 $\begin{array}{ll} r_d \ \underline{=} \ change \ in \ V_{DS} \\ change \ in \ I_D \end{array} \ at \ V_{GS} \ constant \ or \ r_d = V_{DS} \ / \ I_D \ | \ V_{GS} \end{array}$ 

It has a very high value.

### Transconductance, g<sub>m</sub>:

To calculate transconductance determine slope of the transfer characteristics obtained from Observation Table 2

 $g_m \equiv \underline{change \ in \ } I_D \quad at \ V_{DS} \ constant \ or \ r_d = I_D \ / \ V_{GS} \ | \ V_{DS} \ change \ in \ V_{GS}$ 

Its unit is siemens (S) / mho.

#### **Amplification factor, m:**

It is given by

 $\mu = \underline{change in V_{DS}}_{change in V_{GS}} \quad \text{at } I_D \text{ constant or } \mu = V_{DS} / V_{GS} \mid I_{DS}$ 

or  $\mu = g_m * r_d$ 

## DC drain resistance, R<sub>DS</sub> :


It is also called the static or ohmic resistance of the channel. It is given by

 $R_{DS} = V_{DS} \, / I_D$ 

## **Results :**

AC

Drain Resistance r <sub>d</sub>	=
Transconductance,	g <sub>m</sub> =
Amplification factor	μ =
DC drain resistance,	R <sub>DS</sub> =

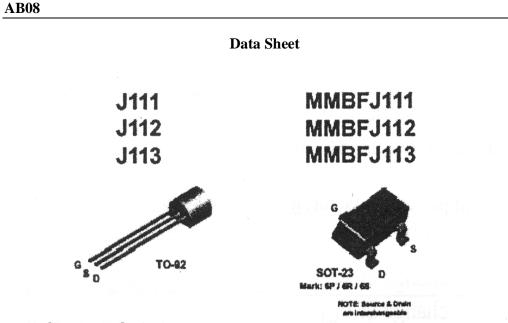

# **N-Channel Switch**

This device is designed for low level analog switching, sample and hold circuits and chopper stabilized amplifiers. Sourced from Process 51.

#### Absolute Maximum Ratings\* YA = 25°C unions of herwise nature

Symbol	Parameter	Value	Units
V	Drain-Gale Voltage	36	V
V.	Gate-Source Voltage	- 35	v
I	Forward Gate Current	50	Acri
T <sub>ar</sub> T <sub>sig</sub>	Operating and Storage Junction Temperature Range	-55 to +150	°C

\*These statege are writing without above which the same trait by of day sees involves or device may be impaired.

#### NOTES

These intergenesis based on a maximum jarchice, temperature of 150 degrees C.
These are steady state term. The factory should be consulted or spheadore eventing putered or torribility systempter.

Symbol	Characteristic		Units	
		J111-113	*MMBFJ111.113	6. S.C.
Po	Total Device Dissipation Densite above 25°C	625 5.0	350 2.8	mW/°C
Raic	Thermal Resistance, Junction to Case	125		"CAV
Rua	Thermal Resistance, Junction to Ambient	\$67	558	"CAV

#### Thermal Characteristics TA-25% unless constants include

\*Device recurring on FR-4 PCB 1.8" X.1.6" X.0.05."

-----

Electrical C	Characteristics	TA = 25*C unitali officiale riskd
--------------	-----------------	-----------------------------------

Symbol	Parameter	Test Conditions	Min	Max	Units

#### **OFF CHARACTERISTICS**

Visitioss	Gate-Source Breakdown Vollage	ka = × 1.0 µA, Vos = 0		• 35		V
loss	Gale Reverse Current	Vas * - 15 V, Vas * 0			- 1.0	nA
Vashin	Gato-Source Cutoff Voltage	Vos = 5.0 V, lo = 1.0 μA	111 112 113	3.0 1.0 0.5	- 10 - 5.0 - 3.0	v v v
latom	Drain Culoff Leakage Current	Vas = 5.0 V, Vas = - 10 V			1.0	nA

#### **ON CHARACTERISTICS**


ion s	Zero-Gate Voltage Drain Current*	Ves = 15 V. les = 0	111	20		mA
			112	5.0		mA
			113	2.0		mA
FD 5(05)	Drain-Source On Resistance	Vos \$ 0.1 V, Vas # 0	111		30	Ω
			112		50	Ω
			113		100	Ω


#### SMALL-SIGNAL CHARACTERISTICS

Cappost Citoront	Drain Gale & Source Gale On Capacitance	V * 0, V * 0, f * 1.0 MHz	28	pF
Capital	Drain-Gate Off Capacitance	Vann # 0, Vann # + 10 V, f # 1.0 MHz	5.0	₽Ë
Cagroft	Source-Gale Off Capacitance	V = 0, V = 10 V, f = 1.0 MHz	5.0	₽F

\*Puter Test Puter With K 200 µK Duty Cyter K 3.0%

# **Typical Characteristics**

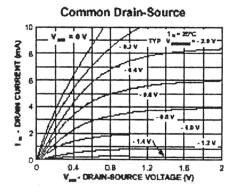

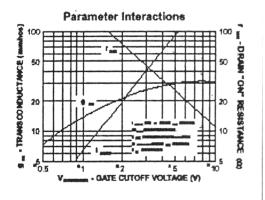

## Warranty

- 1. We guarantee the product against all manufacturing defects for 24 months from the date of sale by us or through our dealers. Consumables like dry cell etc. are not covered under warranty.
- 2. The guarantee will become void, if
  - a) The product is not operated as per the instruction given in the operating manual.
  - b) The agreed payment terms and other conditions of sale are not followed.
  - c) The customer resells the instrument to another party.
  - **d**) Any attempt is made to service and modify the instrument.
- **3.** The non-working of the product is to be communicated to us immediately giving full details of the complaints and defects noticed specifically mentioning the type, serial number of the product and date of purchase etc.
- 4. The repair work will be carried out, provided the product is dispatched securely packed and insured. The transportation charges shall be borne by the customer.

For any Technical Problem Please Contact us at <a href="mailto:service@scientech.bz">service@scientech.bz</a>

#### List of Accessories

1.	2 mm Patch Cords (Red)	. 2 Nos.
2.	2 mm Patch Cord (Black)	. 2 Nos.
3.	2 mm Patch Cord (Blue)	1 No.
4.	e-Manual	1 No.

Updated 08-01-2009